

# Introduction to Electrical Engineering Practice

Course Code: EE 113



Department: Electrical Engineering

Instructor Name: B.G. Fernandes



E-mail id: [bgf@ee.iitb.ac.in](mailto:bgf@ee.iitb.ac.in)





# Diode Rectifier

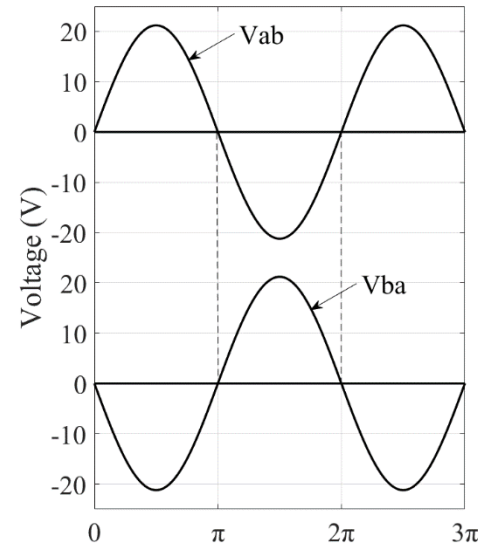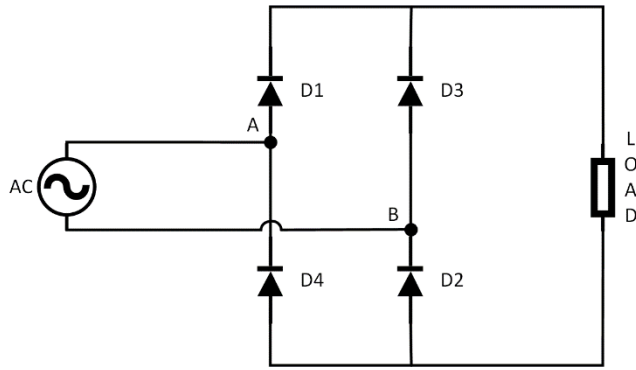

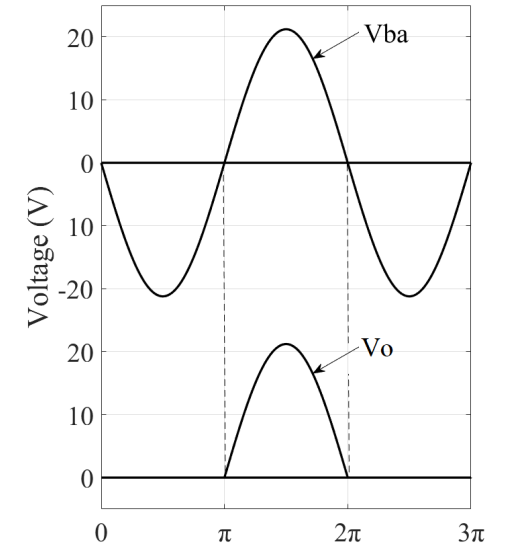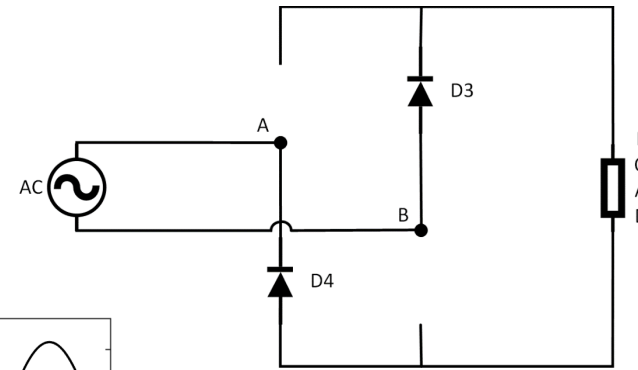
$\pi - 2\pi$   $V_{BA}$  is +ve (Pot of B > Pot of A)



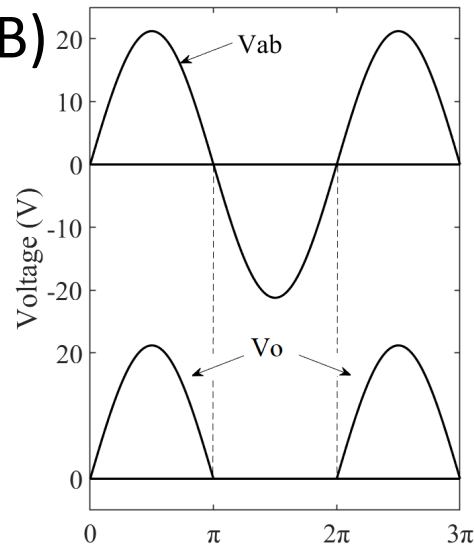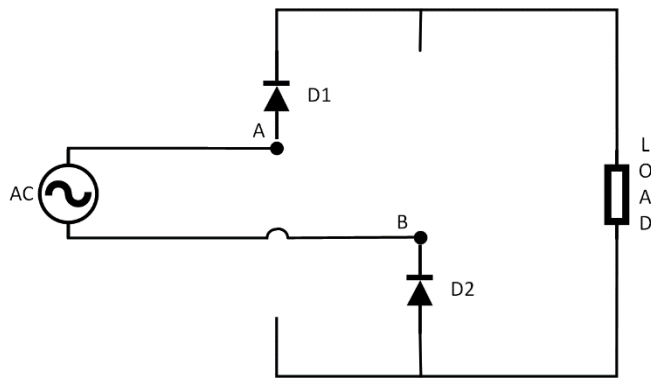$0 - \pi$   $V_{AB}$  is +ve (Pot of A > Pot of B)




# Diode Bridge Rectifier

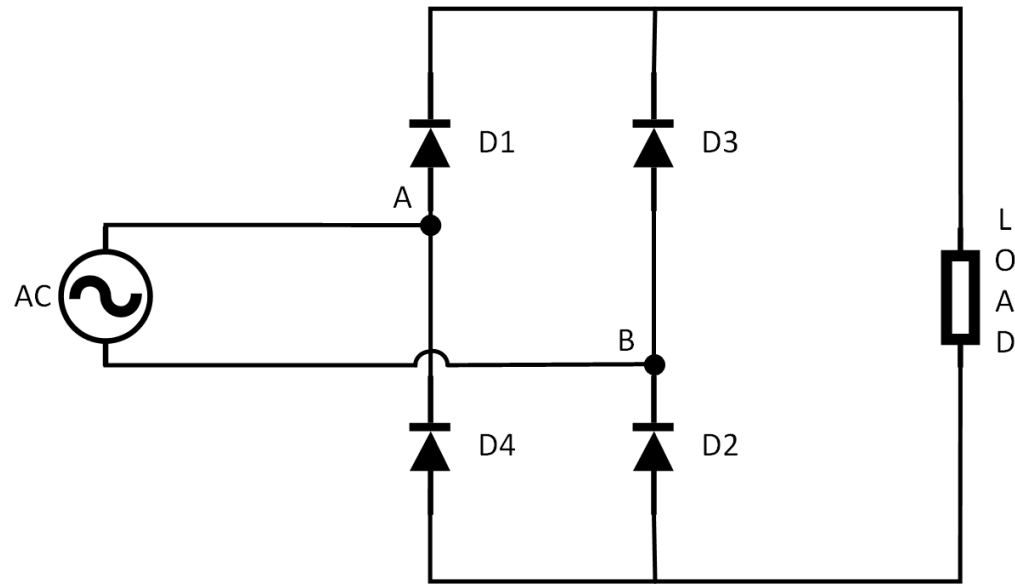

Output Voltage across the load is pulsating and therefore the current.

In case the load requires a constant voltage

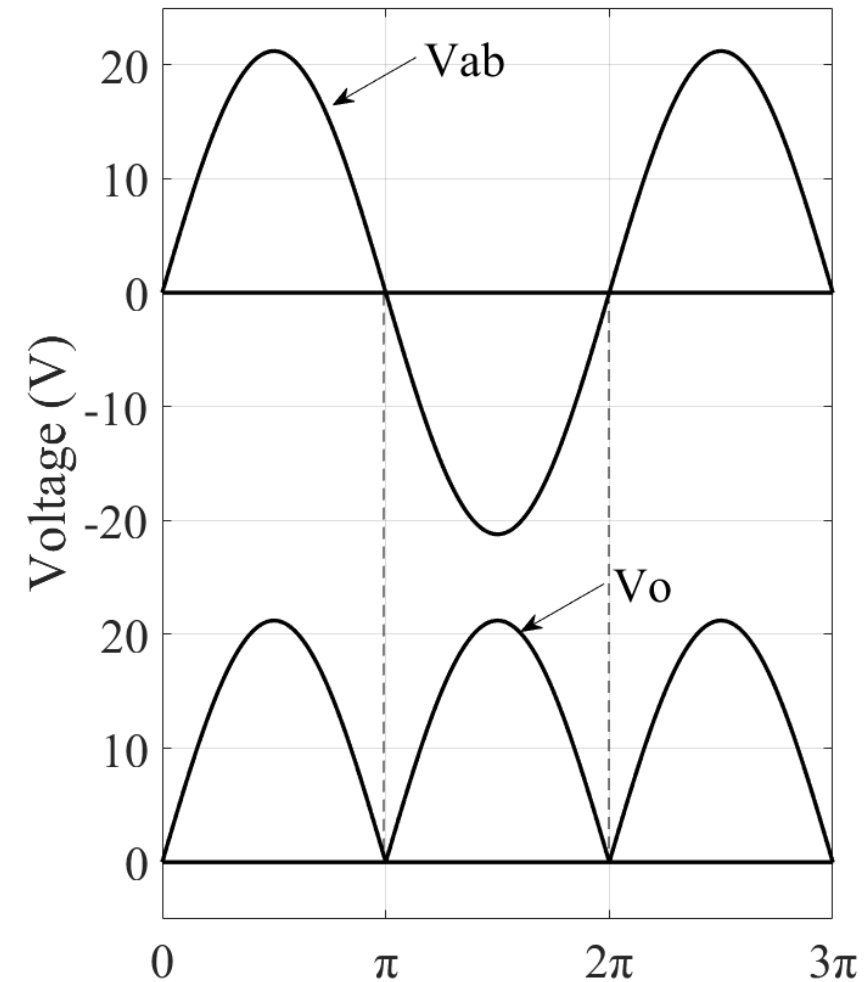- Connect a Capacitor across the load
- $V_o$  should remain  $\approx$  constant.
- Therefore ' $\tau$ ' should be large




# Diode Bridge Rectifier with Capacitor filter

Assume  $V_c = 0$  at  $t = 0$ ;

Switch is closed at  $t = 0$ ;


$D_1 - D_4$  are ideal.

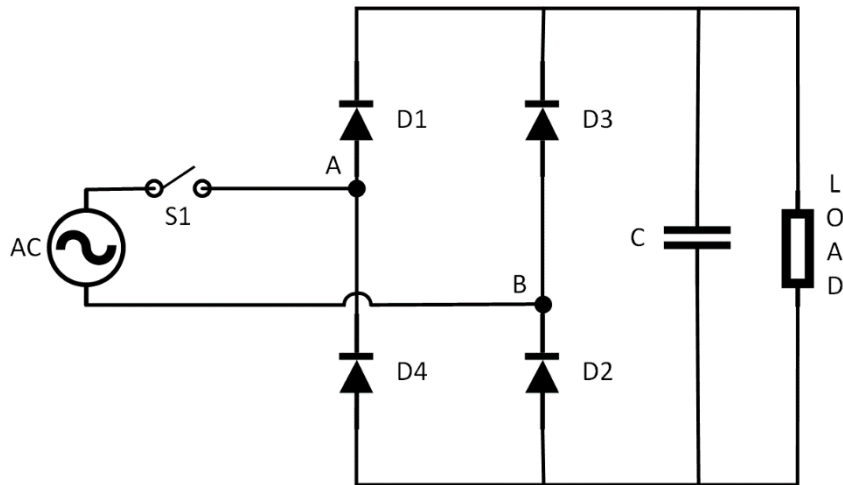

Cathode potential of  $D_1 >$  Anode potential of  $D_1$ .

Diode is Reverse Biased.

Source current = 0

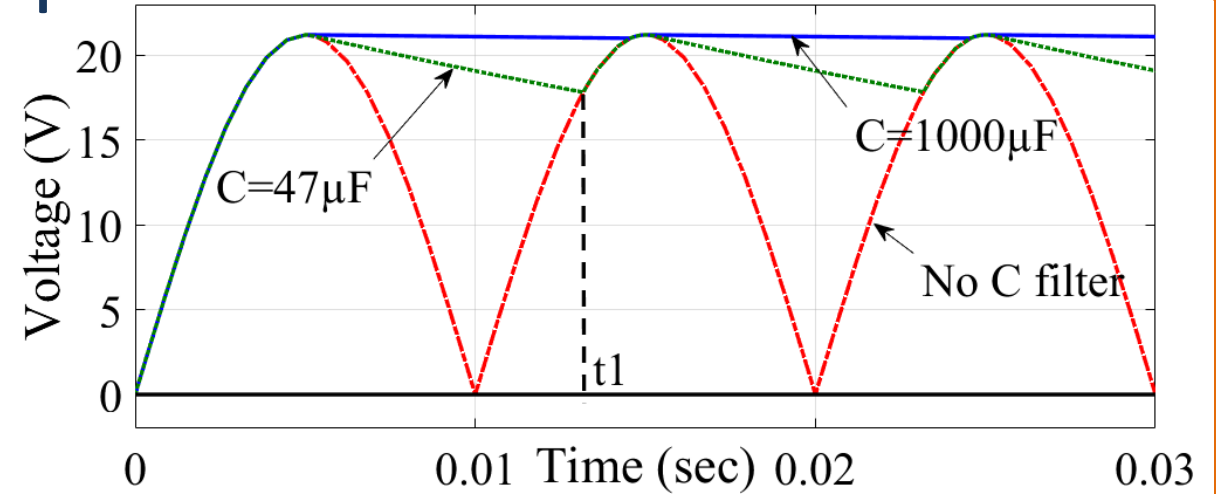


$$V_{AB} = V_o \text{ till } \omega t = \pi/2$$

$$\text{at } \omega t = \pi/2^+$$


$$V_{AB} < V_m \text{ but}$$

$$V_c = V_o = V_m$$


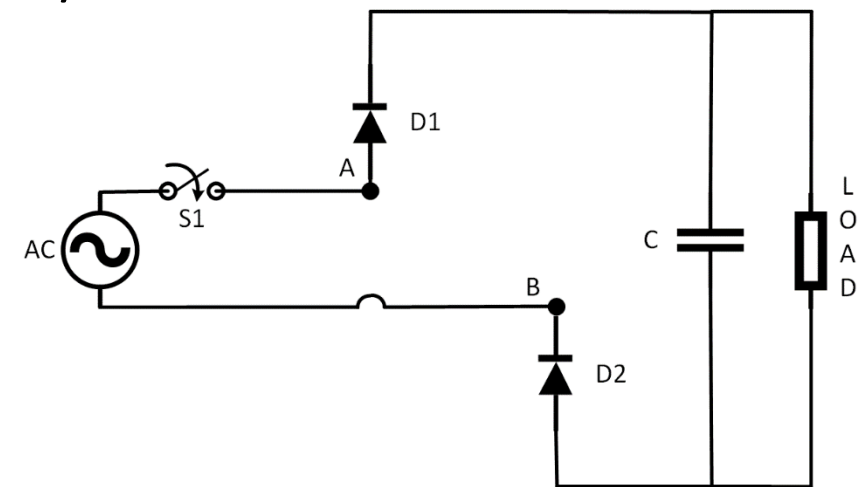

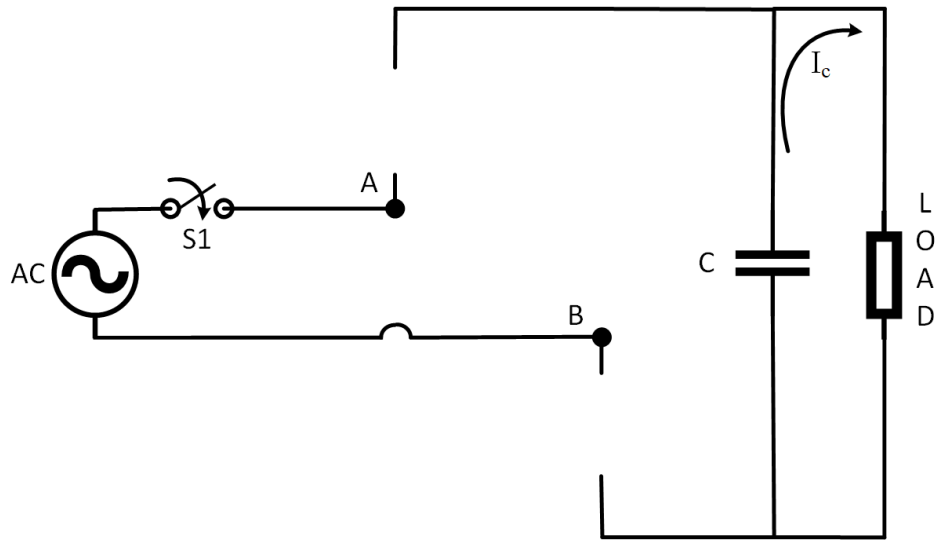
# Diode Bridge Rectifier with Capacitor filter

Source does not supply power.  
Capacitor supplies power to  
the load.



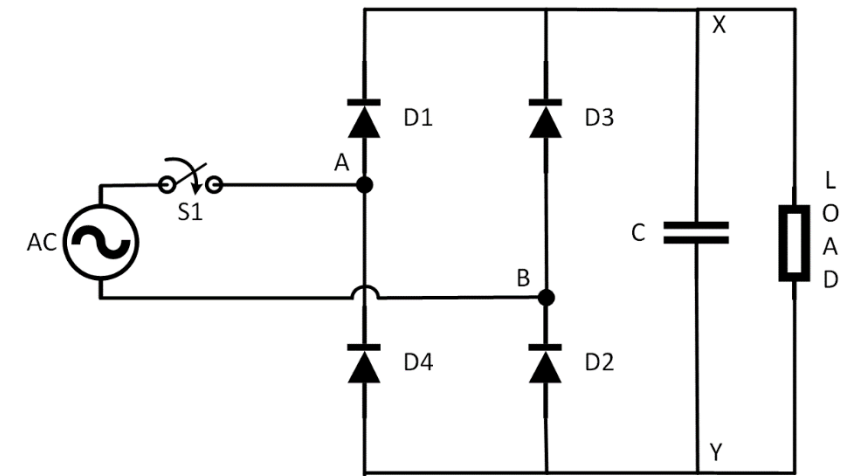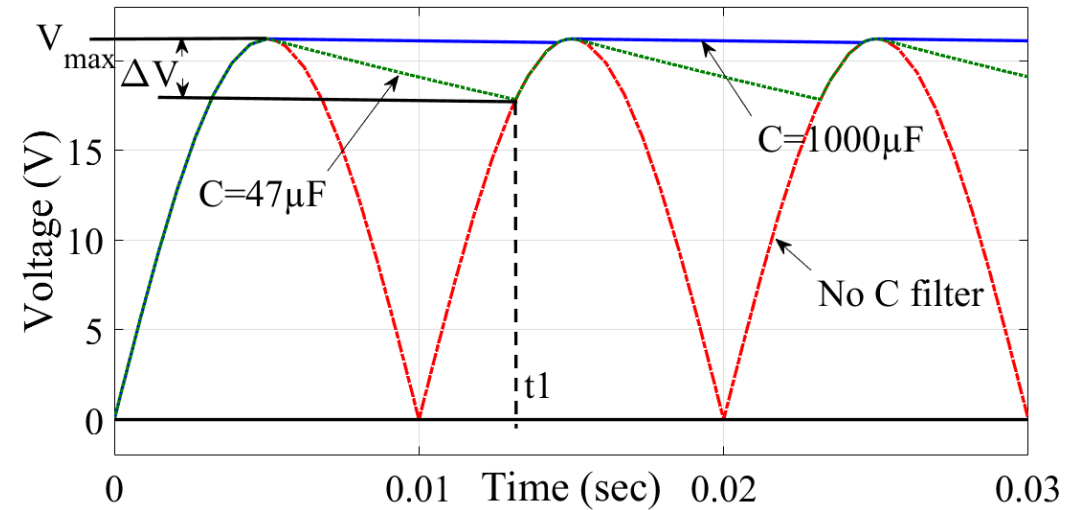Because ' $\tau$ ' is large,  $V_o$  gradually falls, this will continue till  $D_3 - D_4$  starts conducting, this can happen as and when  $V_B > V_X$ .  
It happens at  $t_1$ .



# Unregulated DC Power Supply (using Capacitive Filter)

- Bridge rectifier followed by a large value Capacitor connected parallel to a load resistance


$$C \approx \frac{V_{\max}}{2 * R * \Delta V * f}$$

- Ripple voltage and its reduction
  - Keep on increasing the Capacitor value – not a good solution
  - Use voltage regulator circuits (Zener regulator or Voltage regulator ICs)



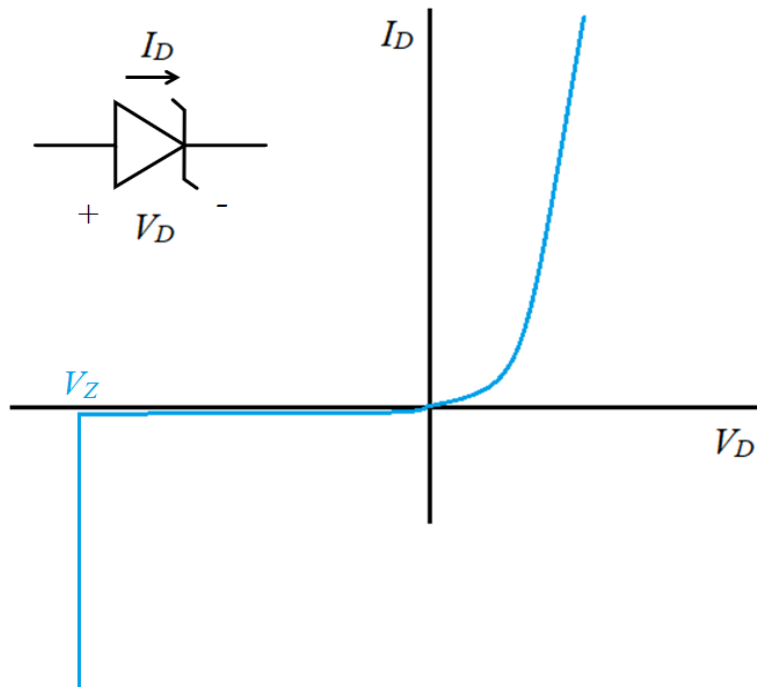
# Zener Diode

- Normal diodes operate in forward biased state, but Zener diode is operated in reverse biased state
- It has very sharp V-I characteristic in reversed direction




Ideal zener characteristics

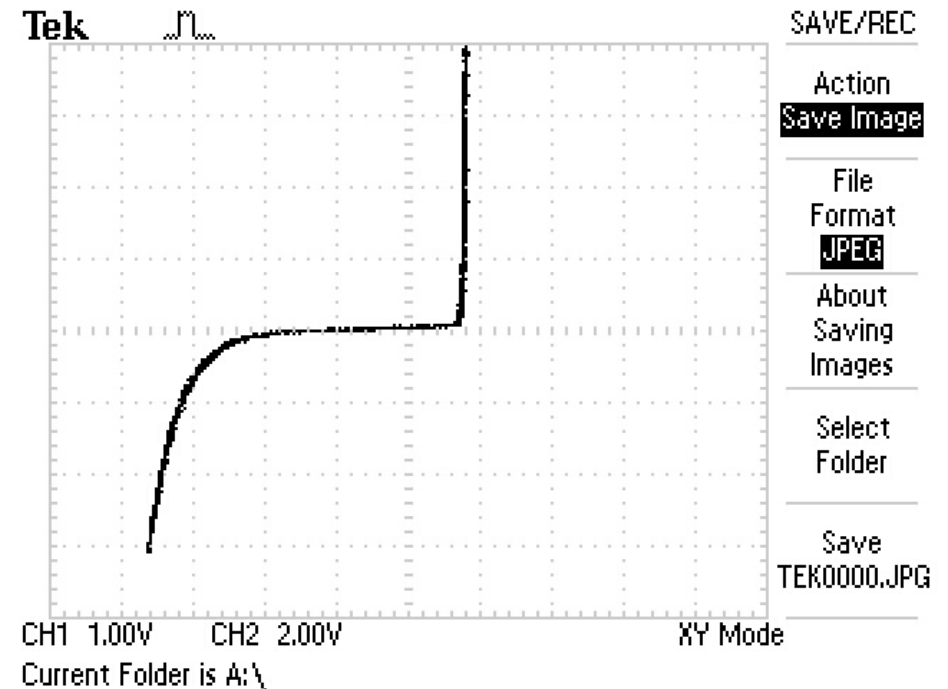

Actual zener characteristics

# Zener Diode as a Voltage Regulator

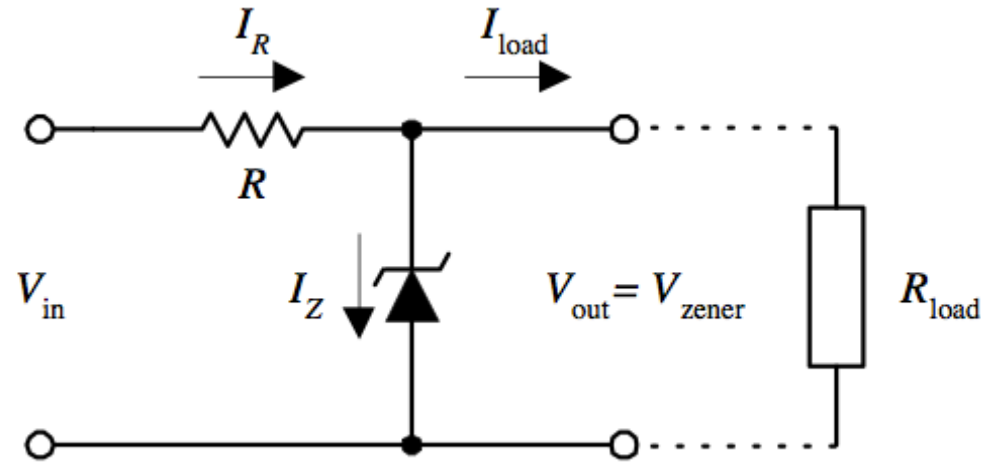



In reverse breakdown range, Zener diode maintains constant voltage across it.

1. Zener diode should be reverse biased and  $R$  should be chosen such that  $I_Z$  should be within its rating.
2.  $I_R = I_{load} + I_Z$





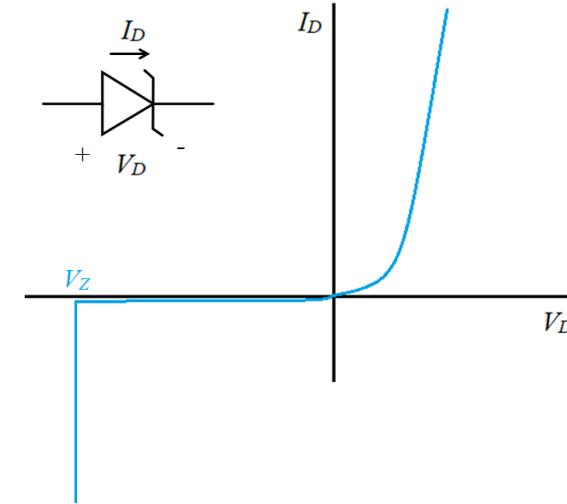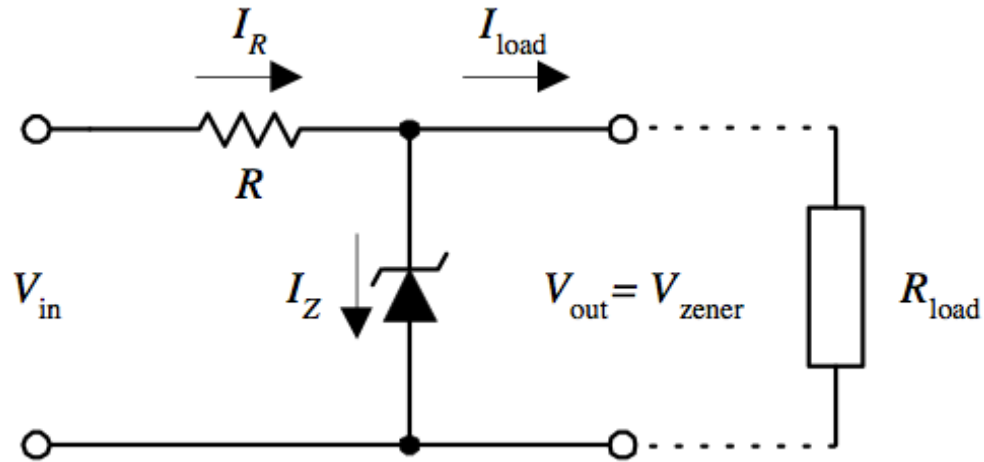
# Zener Diode as a Voltage Regulator (Design)





- Assuming Zener diode to be ideal,  $V_{out} = V_{Zener}$
- Current through  $R$  is  $I_Z + I_{load}$
- When  $I_{load} = 0$  (or  $R_{load}$  is open), Zener diode will have maximum current,
- $I_{Zmax} = \frac{V_{in} - V_{zener}}{R}$
- Choose  $R$  such that  $I_{Zmax}$  is within the permissible range
- For finite values of  $R_{load}$ , load current is,  $I_{Load} = \frac{V_{zener}}{R_{Load}}$





# Zener Diode Clipping Circuits

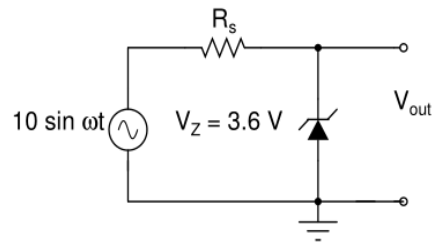

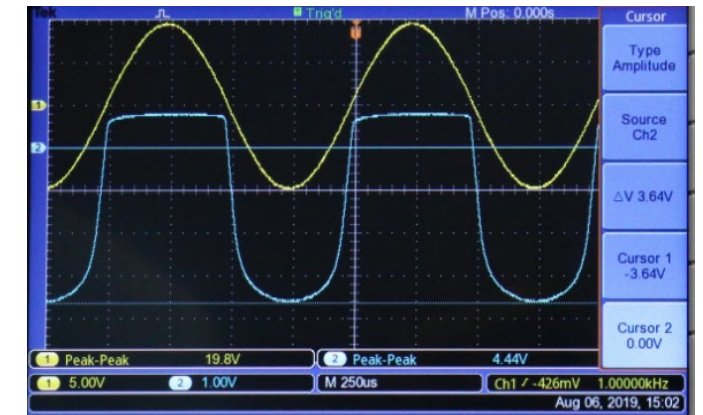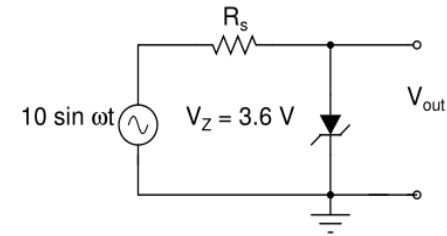Zener diode clipping circuit 1 and the observed  $V_{out}$  waveform



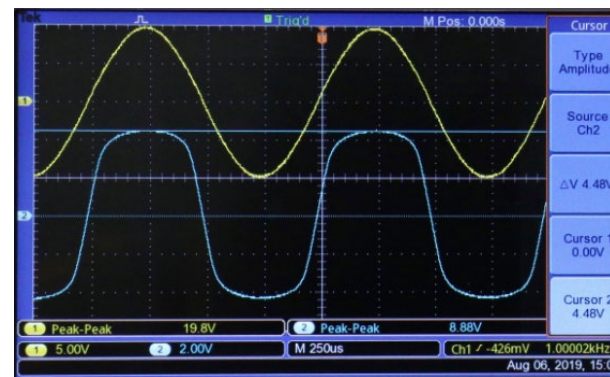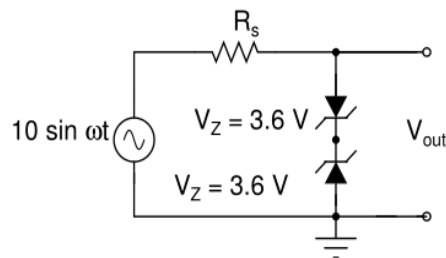Zener diode clipping circuit 2 and the observed  $V_{out}$  waveform



Zener diode clipping circuit 3 and the observed  $V_{out}$  waveform




# Zener Diode as a Voltage Regulator (Design)

- Used for regulating the output voltage of a DC Power supply against variations in the input voltages.
- Effective when the load currents are fairly small. (in the mA range)
- For high currents, voltage regulator ICs are available
  - e.g.: LM7805 5V regulator; LM7812 12V regulator;
  - LM7905 -5V regulator, LM7912 -12V regulator



# Light Emitting Diode (LED)

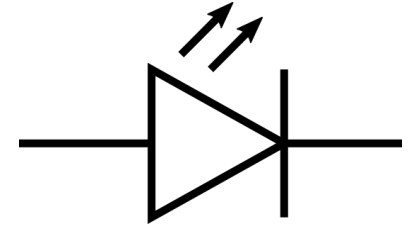


- When electron jumps from conduction band to valence band, it loses energy
- This energy can appear as heat or light
- In silicon, it appears as heat
- In Gallium Arsenide, lost energy appears as light
- When Gallium Arsenide p-n junction is forward biased, it emits light


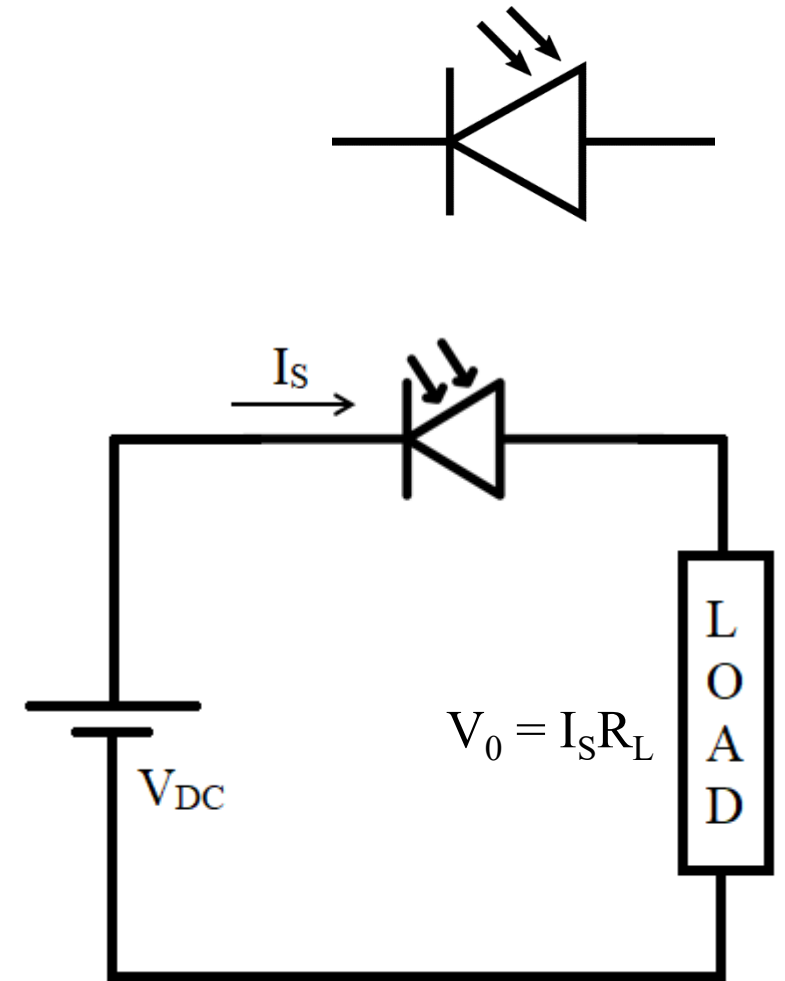
# Photodiode

- Photodiode is operated in reverse biased state
- Functioning is opposite to that of LED
- $I_s$ , reverse saturation current is a function of incident radiation
- When light is incident on the photodiode (junction), electrons absorb energy and jump to conduction band
- Reverse current through the diode increases



# Electric power capacity in India

Total Installed Capacity (31 <sup>st</sup> Oct, 2021)	390.791 GW <sup>†</sup>
Total wind power installations (31 <sup>st</sup> Oct, 2021)	39.990 <sup>†</sup> , (10.23%)
Cumulative solar installations (31 <sup>st</sup> Oct, 2021)	47.665 <sup>†</sup> , (12.19%)

**National Solar Mission** -> **100 GW** Solar Capacity by **2022** <sup>‡</sup>


[†] [https://cea.nic.in/wp-content/uploads/installed/2021/10/installed\\_capacity.pdf](https://cea.nic.in/wp-content/uploads/installed/2021/10/installed_capacity.pdf)

[‡] <https://mnre.gov.in/solar/current-status/>




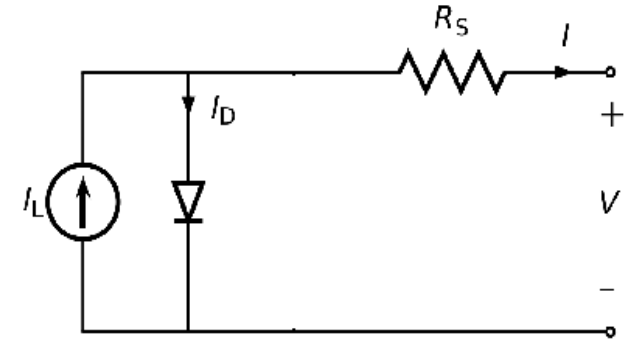
# Diodes vs Solar Cells

- Normal diodes used for rectification are encapsulated in dark epoxy material. Therefore, no light enters the P-N junction.
- Solar cells are also (large area) diodes, but in their case, the junction is intentionally kept bare, (or encapsulated in transparent materials) so that the light enters the P-N junction.
- The light that enters P-N junction of solar cells results in photon-generated current, which is constant for a given light intensity and flows in the opposite direction to that of diode current.
- This current is then passed through the load connected to the solar cell to extract electrical energy from the cell.



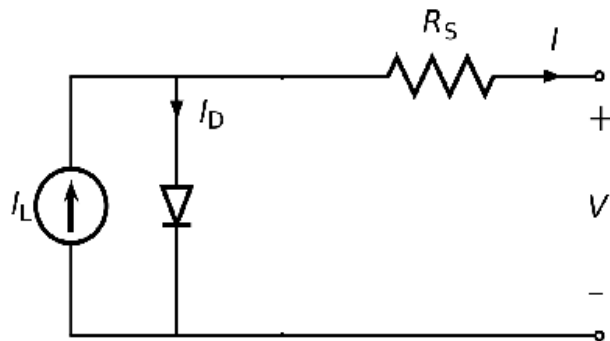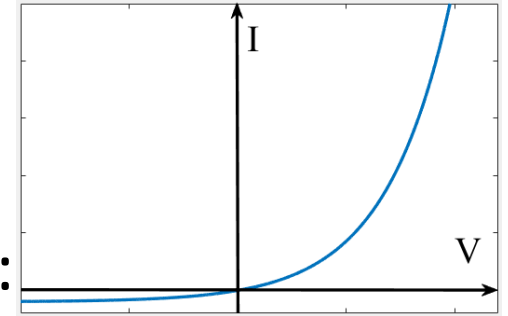
# Current, Equivalent Circuit, I-V Curves


- Diode Current Equation is :  $I = I_s \left( e^{\frac{qV}{kT}} - 1 \right)$
- Considering light generated current in solar cell, it becomes:


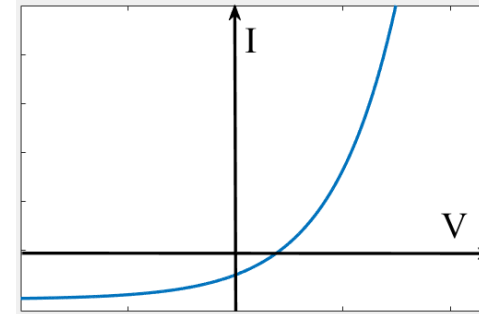
$$I = I_s \left( e^{\frac{qV}{kT}} - 1 \right) - I_L$$




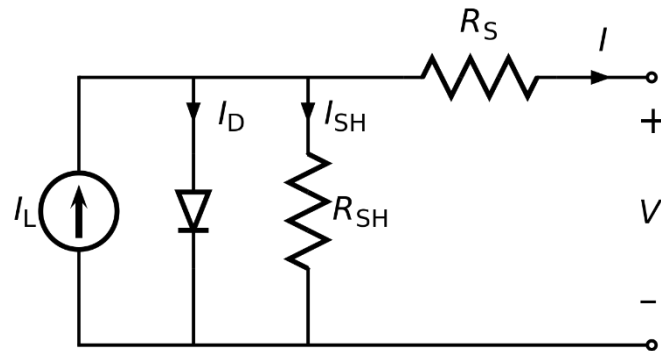*I-V Curve is inverted for convenience. So that we don't have to deal with negative currents*





$$I = I_L - I_s \left( e^{\frac{qV}{kT}} - 1 \right) - \frac{V - IR_S}{R_{sh}}$$

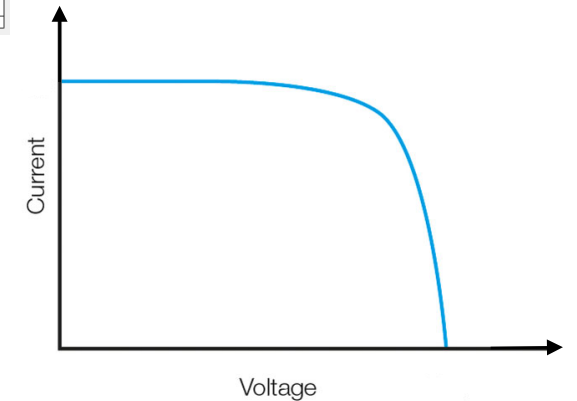$R_{SH} \Rightarrow$  some defects in the solar cell





# Solar cell

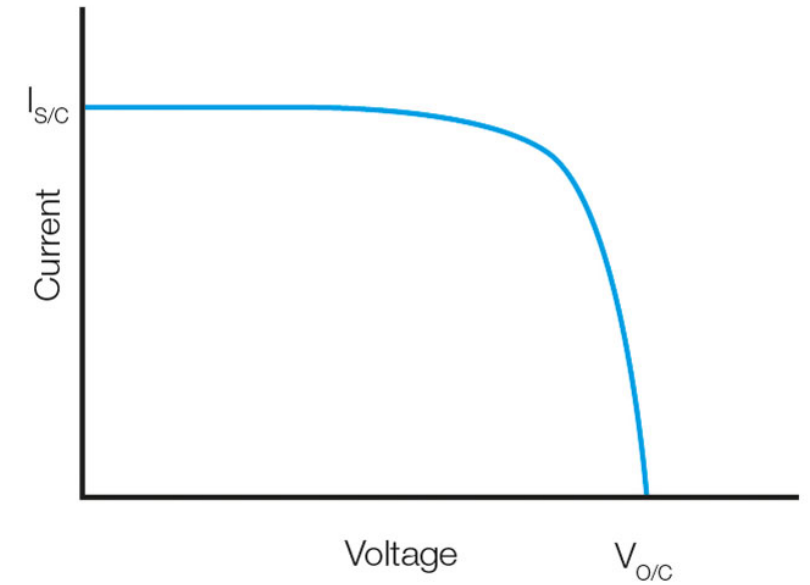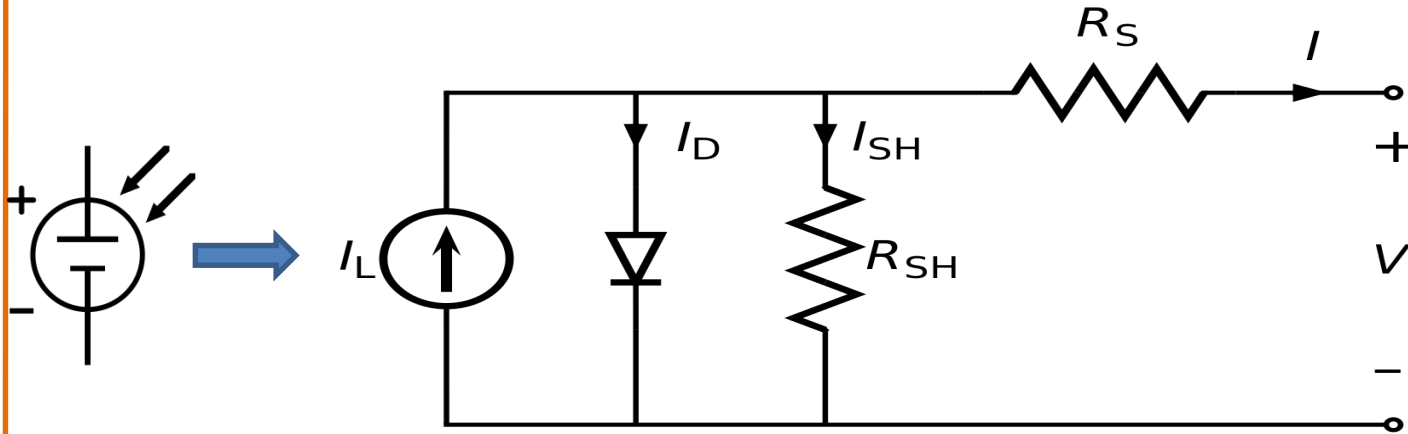

$$I_L = I_D + I_{SH} + I, \quad I_D = I_S e^{\frac{kV_D}{T}} - I_S$$


For a good quality solar cell, its open-circuit voltage ( $V_{OC}$ ) and short-circuit current ( $I_{SC}$ ) are given as follows

$$V_{OC} \approx \frac{nkT}{q} \ln \left( \frac{I_L}{I_S} + 1 \right)$$

$$I_{SC} = I_L$$





# Solar Cell Characteristic

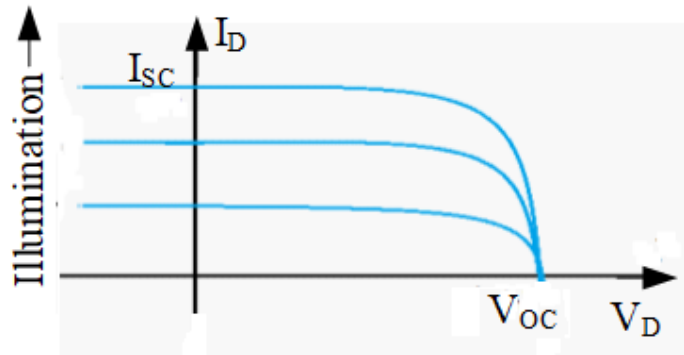

Effect of illumination intensity on V-I characteristic

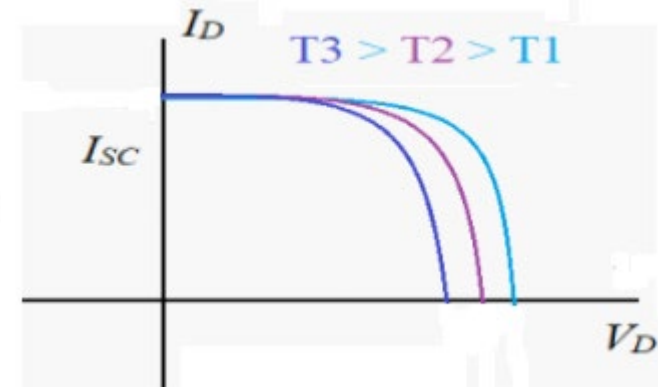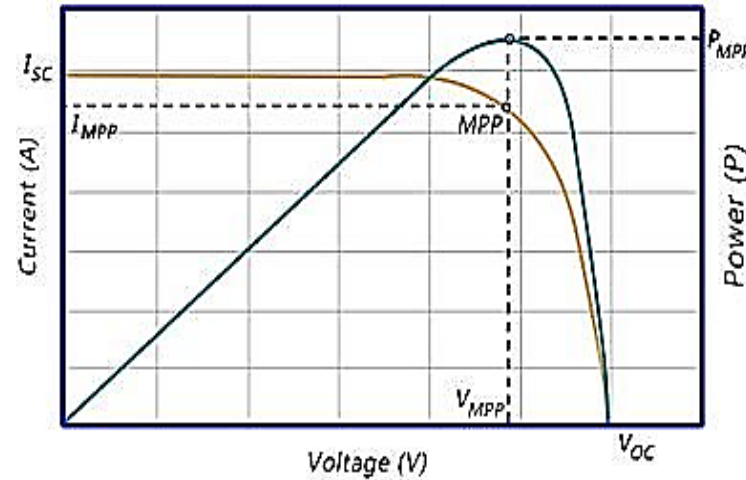- Illumination intensity affects  $I_{sc}$
- Temperature affects  $V_{oc}$





Effect of temperature on V-I characteristic

# Transistor


**Diode:** 2 terminal device → Uncontrolled Switch → Device starts conducting when  $V_{AK} > 0.7 \text{ V}$

**Transistor:** 3 terminal device → Controlled Switch → Two types.



## PNP Transistor

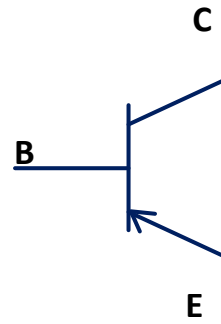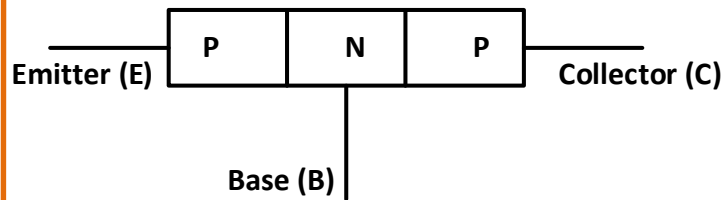

$$V_{BB} = V_{BE} + i_B R_B$$

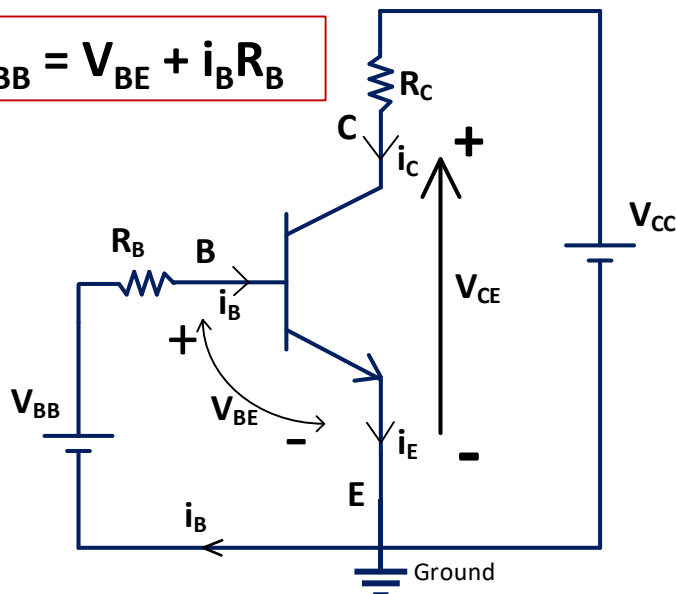

## NPN Transistor

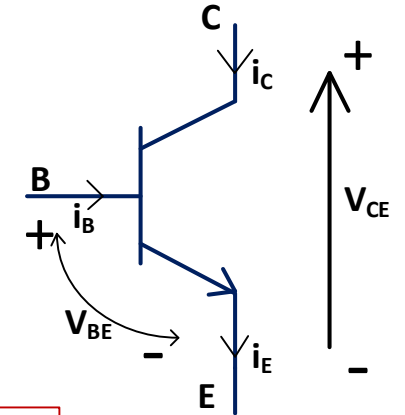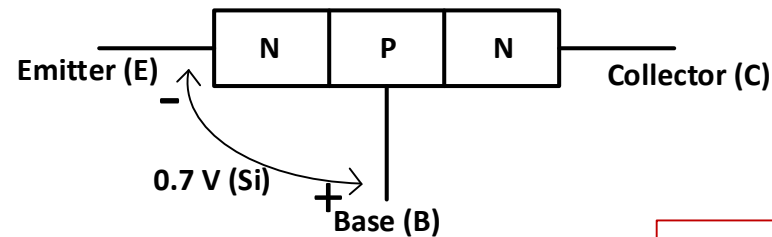

$$I_E = I_C + I_B$$

When  $V_{BE} < 0.7$ ; Transistor is off → "Cut-off"

In **ON state**, there are TWO modes.

**Active :**  $I_C = \beta I_B$ ; where  $\beta = h_{FE}$  = current gain →  $\gg 1$

$$V_{CE} = V_{CC} - i_C R_C > V_{CE(Sat)}$$

$$\min(V_{CE}) = V_{CE(Sat)} \approx 0.2 \text{ V}$$

**Saturation :**

$$I_C \neq \beta I_B ; \quad i_C = \frac{V_{CC} - V_{CE(Sat)}}{R_C}$$




# Transistor

## Conclusions:

- When  $V_{BE} < 0.7$ ; Transistor is off  $\rightarrow$  “**Cut-off**” mode
- In **Active** region,  $I_C = \beta I_B$ ;  $V_{CE} = V_{CC} - i_C R_C$   $\rightarrow$  used as an **AMPLIFIER**
- In **Saturation** region,  $i_C = \frac{V_{CC} - V_{CE(Sat)}}{R_C}$   $\rightarrow$  used as a **SWITCH**
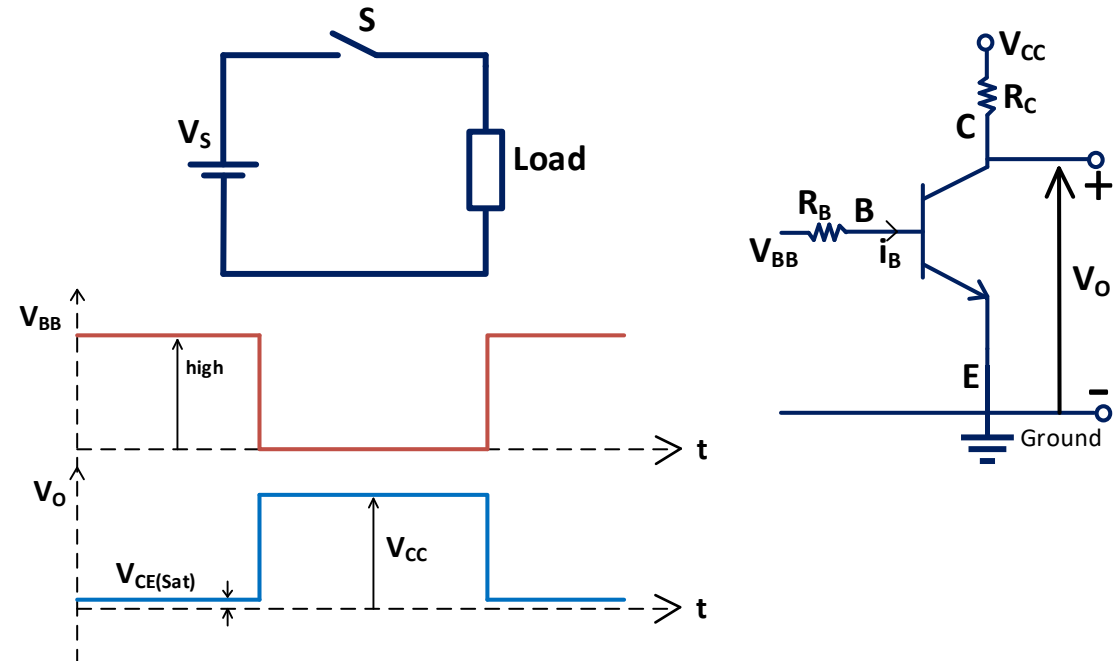
## As a Switch:

- When OFF, voltage across switch =  $V_s$
- When ON, voltage across switch =  $0 \approx V_{CE(Sat)}$
- Assumed that resulting  $i_B$  saturates the transistor
- $V_O$  = voltage across the transistor ( $V_{CE}$ ) is the complimentary of the signal applied at the base circuit  $\rightarrow$  **INVERTER**



# Transistor

