

EE114 POWER ENGINEERING 1

ASSIGNMENT - 1

- SATHVIK KANNA

210070077

Question 1)

$$v = 100 \cos(240\pi t + 45^\circ) \text{ mV}$$

$$1) f = \frac{\omega}{2\pi} \Rightarrow \frac{240\pi}{2\pi} \Rightarrow \boxed{120 \text{ Hz}}$$

$$2) \text{Time period} = \frac{1}{f} = \frac{1}{120} = \boxed{8.3 \text{ ms}}$$

$$3) V_{\max} = \boxed{100 \text{ mV}}$$

$$4) v(0) = 100 \cos(45^\circ) = \boxed{70.71 \text{ mV}}$$

$$5) \phi = 45^\circ / \frac{\pi}{4} \text{ radians}$$

$$6) v = \text{zero when } (240\pi t + 45^\circ) = \frac{\pi}{2}$$

$$\therefore 240t + \frac{1}{4} = \frac{1}{2} \Rightarrow t = \frac{1}{960} = \boxed{1.04 \text{ ms}}$$


$$7) \frac{dv}{dt} = -100 \cdot 240\pi \sin(240\pi t + 45^\circ) \text{ mV}$$

$$\frac{dv}{dt} = 0 \text{ when } 240\pi t + \frac{\pi}{4} = \pi$$

$$t = \frac{3}{960} = \boxed{3.125 \text{ ms}}$$

Question 2)

$$v = 60 \cos(\omega t + \phi)$$

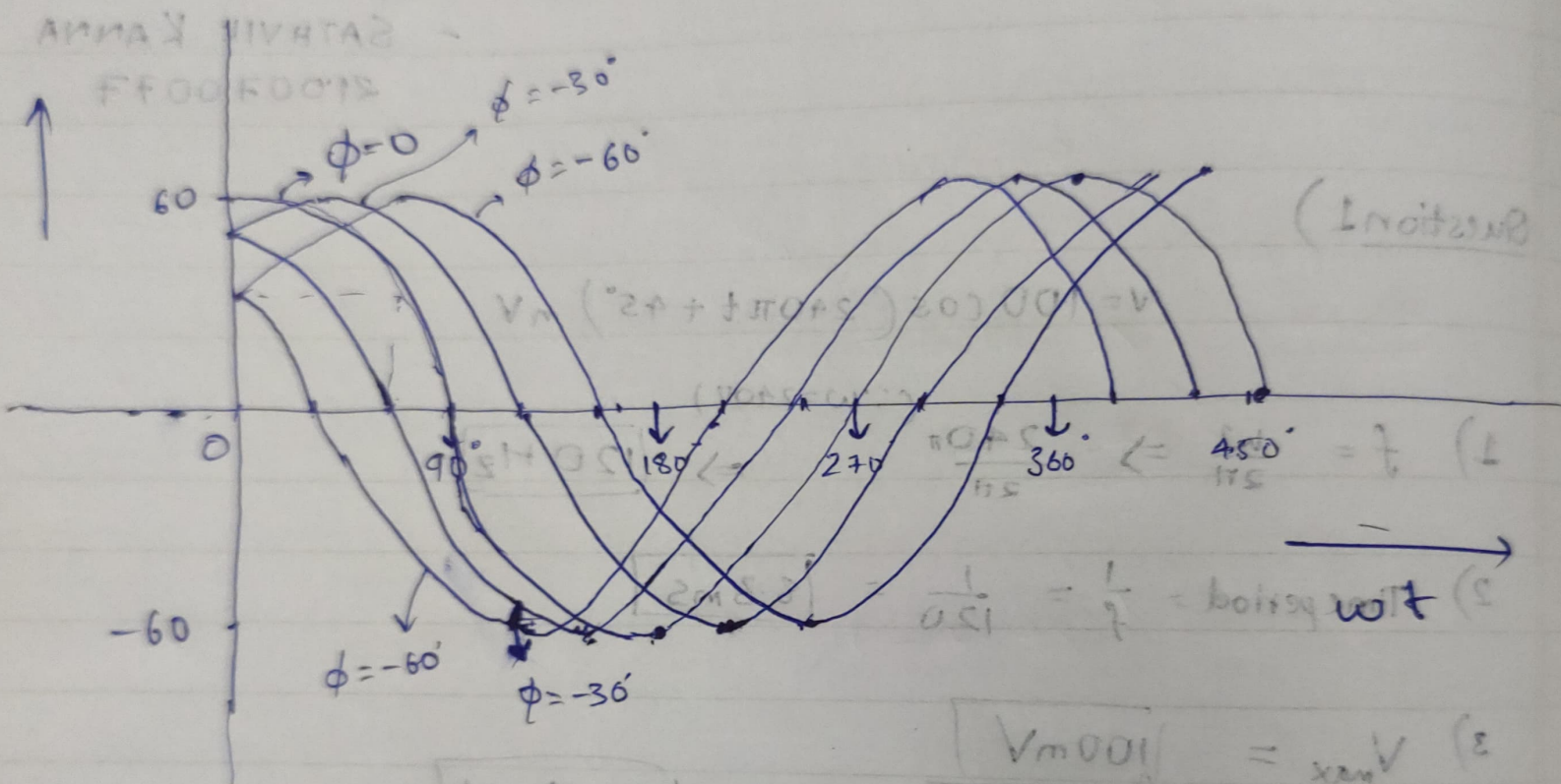

1) AS ϕ becomes more positive the function shifts towards left.

2) as ϕ changes from 0 to -30° the graph shifts rightwards

⑧ Question 3

$$v(t) = 170 \cos(120\pi t - 60^\circ)$$

1.) maximum value of voltage is 170V

2) frequency = $\frac{\omega}{2\pi} \Rightarrow \frac{120\pi}{2\pi} = 60\text{Hz}$

3) $\omega = 120\pi$ rads per second.

4) phase angle in radian = $-\pi/3$

5) phase angle in degrees = -60°

6) period = $\frac{1}{f} = 16.66\text{ms}$

7) $v = 170$ when $120\pi t - \frac{\pi}{3} = 0 \Rightarrow t = \frac{1}{360} = 2.77\text{ms}$

8) expression is $170 \cos\left(120\pi\left(t - \frac{125}{18000}\right) - 60^\circ\right)$

$\Rightarrow 170 \cos(120\pi t - 1.16\pi)$


9) the function should be shifted $T - 2.77\text{ms}$ to right

$\Rightarrow 13.89\text{ms}$

10) the function should be shifted 2.77 ms to left.

Question 4)

1.)

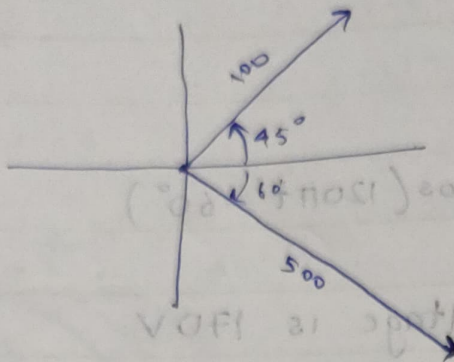

$$x \text{ component} = 250 + 50\sqrt{2}$$

$$y \text{ component} = 50\sqrt{2} - 250\sqrt{3}$$


$$\omega = 300$$

$$\Rightarrow \sqrt{(x_{\text{comp}})^2 + (y_{\text{comp}})^2} = \text{Amplitude} \Rightarrow \underline{483.85}$$

$$\text{phase} = \tan^{-1}\left(\frac{y_{\text{comp}}}{x_{\text{comp}}}\right) \Rightarrow \underline{-48.48^\circ}$$

$$\Rightarrow \underline{483.85 \cos(300t - 48.48^\circ)}$$

2.)

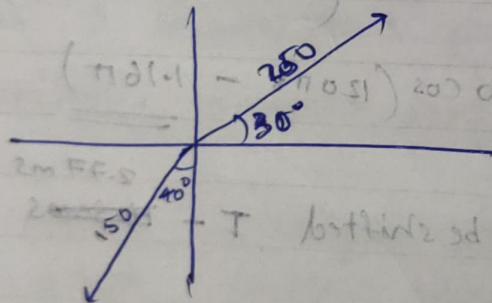

$$x \text{ component} = 120.08$$

$$y \text{ component} = 10.09$$

$$-150 \sin(377t + 140) \Rightarrow -150 \cos(377t + 50^\circ)$$


$$\Rightarrow \underline{150 \cos(377t - 130^\circ)}$$

$$\text{Amplitude} = \sqrt{(x^2) + (y^2)} = 120.42$$

$$\text{phase} = \tan^{-1} \frac{y}{x} = 4.80^\circ$$

$$\Rightarrow \underline{120.42 \cos(377t + 4.80^\circ)}$$

3)

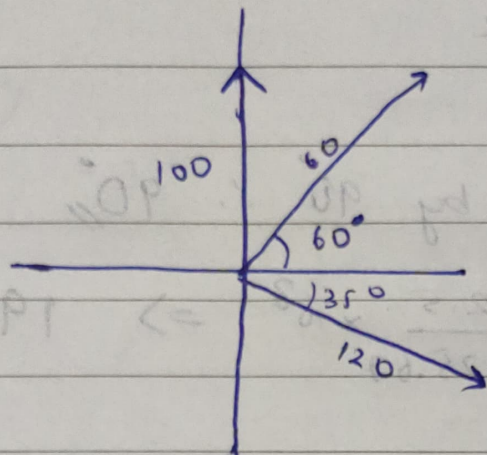

$$x_{comp} = 128.29$$

$$y_{comp} = \cancel{16.86}$$


$$83.014$$

$$Amp = 152.88$$

$$Phase = 32.94^\circ$$

$$\Rightarrow 152.88 \cos(100t + 32.94^\circ)$$

4)

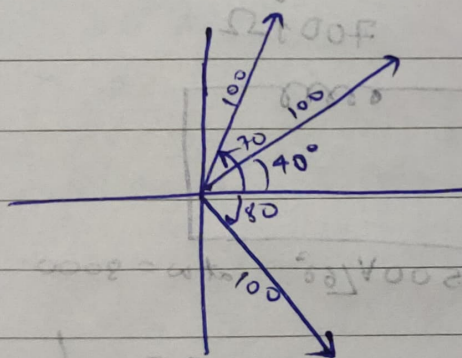

$$x = 100 \cos 70 + 100 \cos 40 + 100 \cos 80$$

$$y = 100 \sin 70 + 100 \sin 40 - 100 \sin 80$$

$$\therefore 141.42 \cos(\omega t + 25^\circ)$$

Question 5

$$v = 2.5 \cos(\omega t) \text{ mV}$$

$$\omega = 2\pi \cdot 40 \times 10^3$$

① $\omega \Rightarrow 80\pi \times 10^3 \text{ rad/sec}$

② current leads voltage by $90^\circ \therefore 90^\circ$


③ $\frac{V}{I} = X_c \Rightarrow \frac{2.5 \times 10^{-3}}{125.67} \Rightarrow 19.89$

④ $\frac{1}{C\omega} = 19.89 \therefore C = \frac{1}{19.89 \times 80\pi \times 10^3} = 2 \times 10^{-7} = 0.2 \mu\text{F}$


⑤ $-19.89j$

Question 6

1)

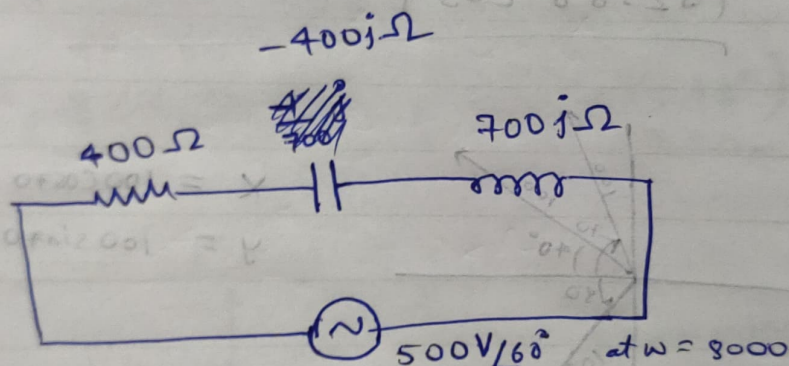

2)

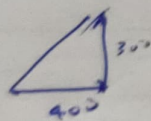

$$\tan^{-1} \frac{3}{4} = 36.87^\circ \therefore 60 - 36.87 = \underline{\underline{23.13^\circ}}$$


3)

$$I = 1 \angle 23.13^\circ$$

4)

$$i(t) = 1 \cdot \cos(8000t + \cancel{36.87}^{23.13})$$

Question 7

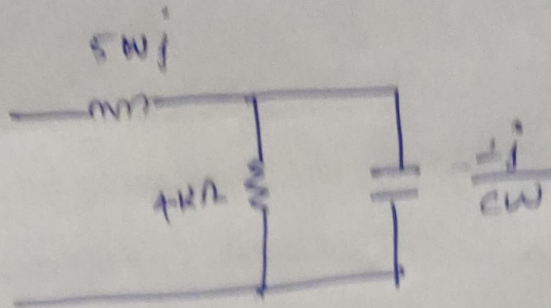

$$Lj\omega + \frac{-Rj\omega}{c\omega} = \frac{R - \frac{j}{c\omega}}{1}$$


$$\Rightarrow 5\omega = \frac{16 \times 10^5}{\omega^2 + 16 \cdot 10^4}$$

$$\omega^2 + 16 \cdot 10^4 = 32 \times 10^4$$


$$1) \quad \omega = 400 \text{ rad/sec}$$


$$2) \quad \frac{64 \times 10^4}{32 \times 10^4} = 2 \text{ k}\Omega$$

Question 8

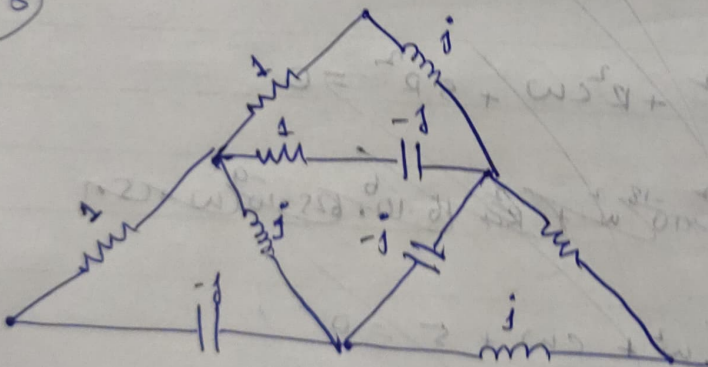


$$\frac{(1+j)(1-j)}{2} = 1 \Omega$$

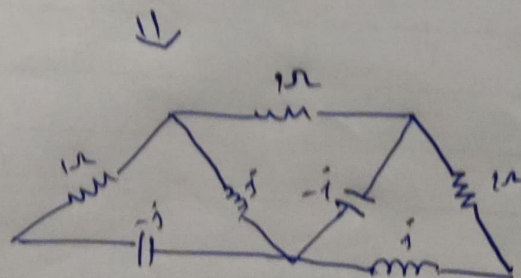

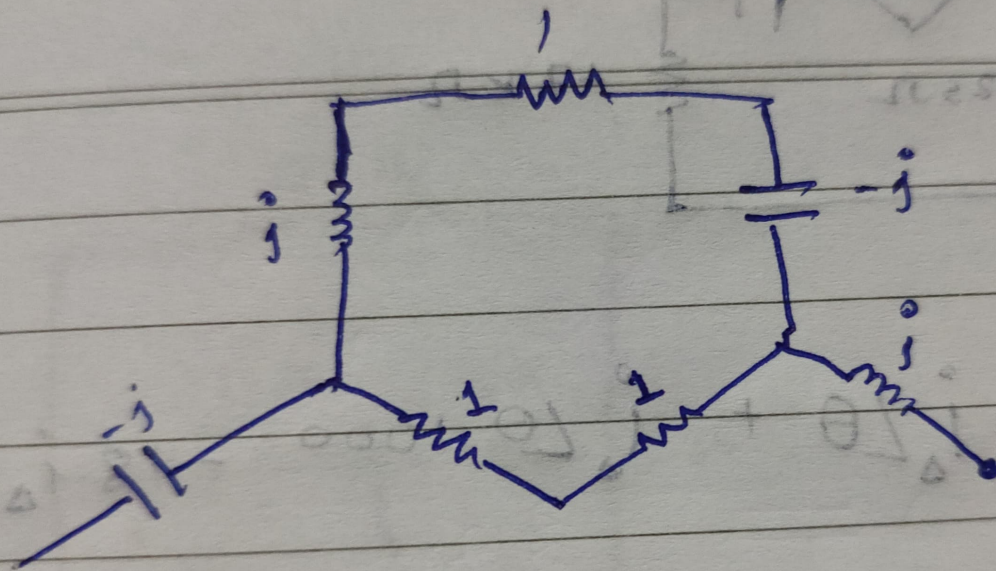

$$\Rightarrow \frac{2}{3} \Omega$$


10

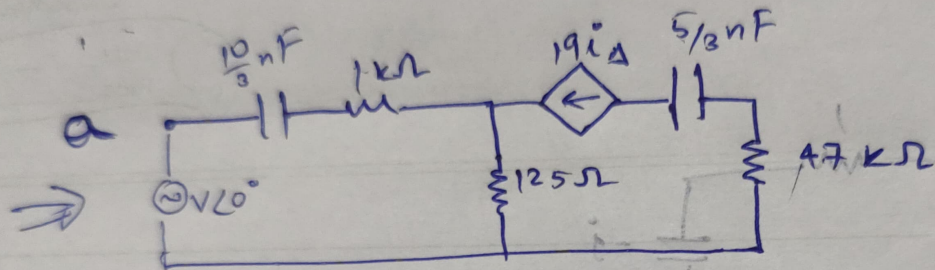

$$v_{L0} = -j12000 \times i_\Delta \angle 0^\circ + i_\Delta \angle 0^\circ \times 1000 - 18 i_\Delta \angle 0^\circ \times 125$$

$$Z_{ab} = \frac{v_{L0}}{i_\Delta \angle 0^\circ} = -j \times 12000 - 1250$$

$\Omega \frac{5}{8}$

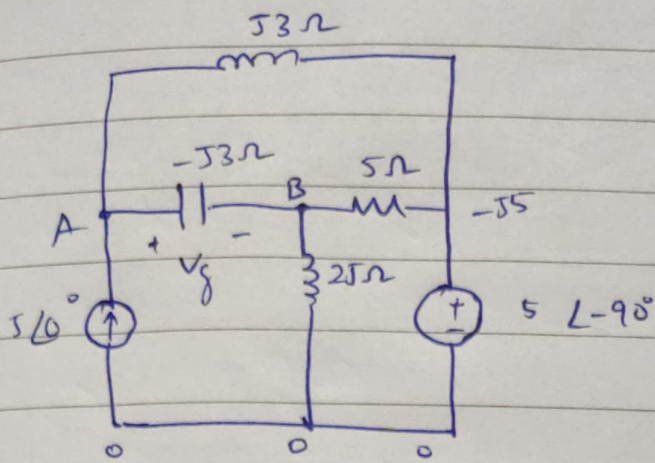

CLL

$$5 = \frac{V_A + j5}{j3} + \frac{V_A - V_B}{-j3}$$

$$\frac{V_B}{j2} + \frac{V_B + j5}{5} + \frac{\cancel{V_B} + j3}{-j3} \frac{V_D - V_A}{-j3} = 0$$

$$j15 = \cancel{V_A} + j5 + V_B - \cancel{V_A}$$

$$\boxed{V_B = j10}$$

$$\Rightarrow 5 + 3j + \frac{j10 - V_A}{-j3} = 0$$

$$-15j + 9 + j10 - V_A = 0$$

$$\boxed{V_A = -j5 + 9}$$

$$\boxed{V_A - V_B = -j15 + 9}$$