

# Introduction to Electrical Engineering Practice

Course Code: EE 113

Department: Electrical Engineering

Instructor Name: B.G. Fernandes

E-mail id: [bgf@ee.iitb.ac.in](mailto:bgf@ee.iitb.ac.in)



# Introduction to the Course

- Covers various aspects of Electrical and Electronics Engineering
  - basic circuits to control systems.
- Main objective:
  - to motivate EE students to pursue further studies and a career in EE.
- Involves practical aspects of day-to-day Electrical/Electronics engineering in our lives.
- Will have demonstration of experiments to reinforce classroom learnings.



# Five Modules

- Analog Electronics
- Digital Electronics
- Signals & Systems
- Energy Systems
- Control systems



## Marks Distribution(Tentative):

First mid-semester exam	25%
End Semester exam	45%
Laboratory	20%
Quiz	10%

### Plan:

One Quiz per module

Midsem and End sem examinations



# Broad outline and plan

- Five lectures per module – Total of 26 lectures
- Two lab experiments per module – 10 experiments
- Timings:
  - Lectures: Monday 9:30-10:25 Hrs and Tuesday 10:35-11:30 Hrs
  - Tutorial: Thursday 10:35-11:30 Hrs
  - Lab Demos: Thursday 11:35-12:30 Hrs
  - Doubt clearing session 5:00-6:00 PM from 8<sup>th</sup> December



# Reference Material

- Reference material
  - Will be uploaded on Moodle and Teams
- Home Practice problems will also be uploaded



# Remember..

`Not everything that counts can be counted  
and not everything that is counted truly counts'

Create a meaningful purposeful fulfilling lives for yourselves and  
learn how to use that to make an impact and a difference in the lives  
of others..





- Day in the life of hibiscus mutabilis aka China rose/Confederate rose/Bettada Tavare/Neladavare. It is pure white in the morning when it blooms and slowly turns pink as the sun comes up and is bright pink by sunset.
- Here is a series of pictures taken at 6:30 am, 8:30 am, 11:30 am and 6:00 pm. Wonderful creation of nature.





- The sun has set and I have done my bit to add beauty and colour to the world I existed in, although just for a day.

Finally,  
‘They can because they think they can...’  
Good luck to all of you....



# Analog Electronics: Syllabus


- KCL, KVL fundamentals, network theorems
- PN diodes, and other special diodes, transistors
- Opamp Circuits




# Review of DC Circuit Analysis & Network Theorems:

Electric Circuit  $\Rightarrow$  Closed path composed of active & passive elements.

Active Elements  $\Rightarrow$  Capable of delivering power to some external device

Two types 


- Independent source
- Dependent source

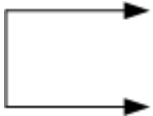Independent source 


- Independent V source
- Independent I source



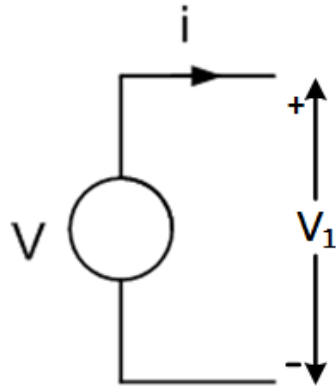
Independent  $V$  source  $\longrightarrow$  Terminal  $V$  is INDEPENDENT of  $I$  flowing through it.



Ideal

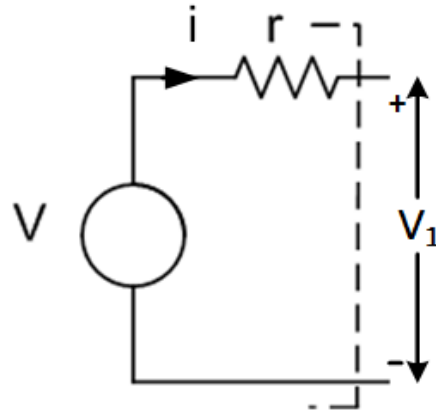

Non-ideal

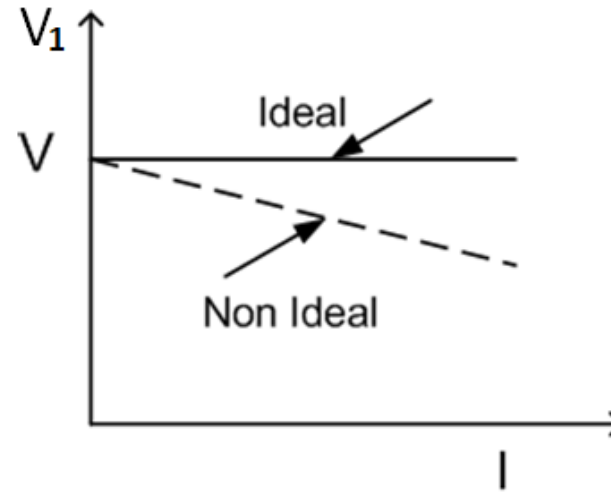

$\Rightarrow$  Battery




- Ideal  $V$  source can “source and sink” any current within its rated value
- Current through  $V$  source can change instantaneously

Precautions:

- Never **short-circuit** a  $V$  source
- Do not connect two  $V$  sources of **different magnitude in parallel**



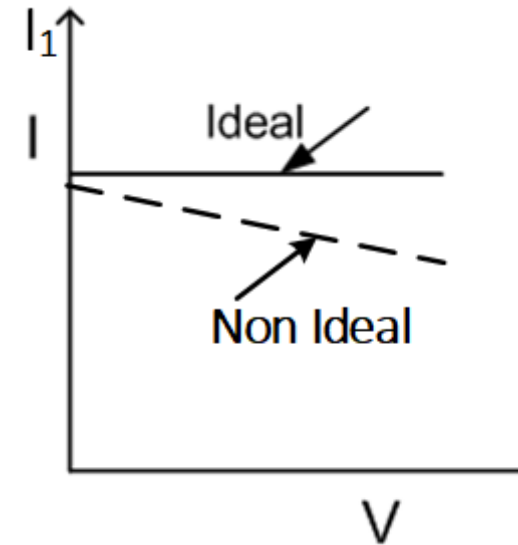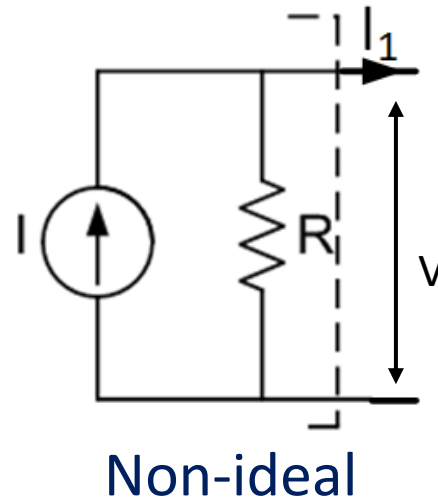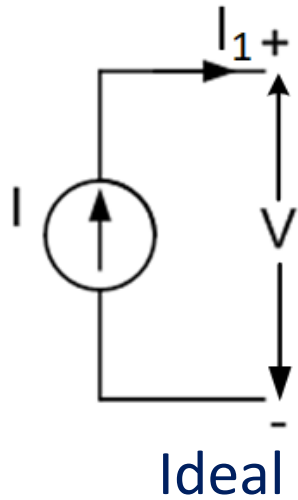Independent I source : I is independent of 'V' across it




- Ideal I source can have any voltage across it (within its rated value)
- Voltage across the I source can change instantaneously

Precautions:


- Never **open-circuit** a I source
- Do not connect two I sources of **different magnitude in series**



## How to realize a current source??

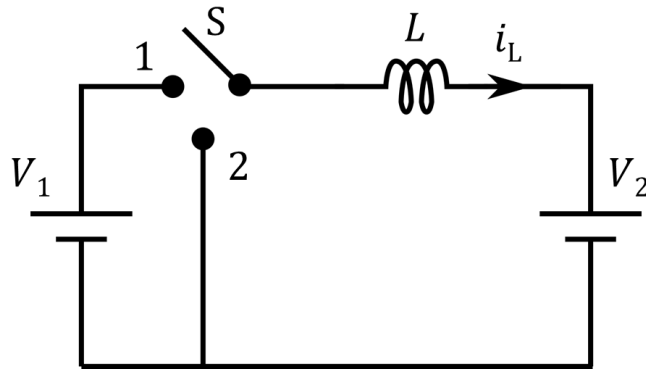


$$V_1 > V_2$$

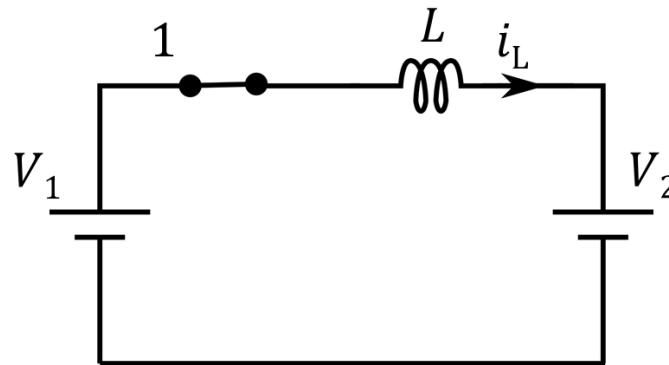


When S at position 1
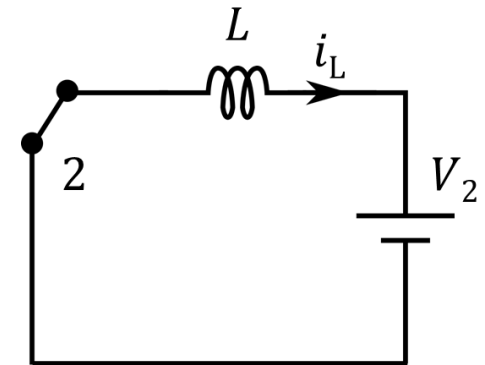
$$di_L = \left( \frac{V_1 - V_2}{L} \right) dt$$




When S at position 2
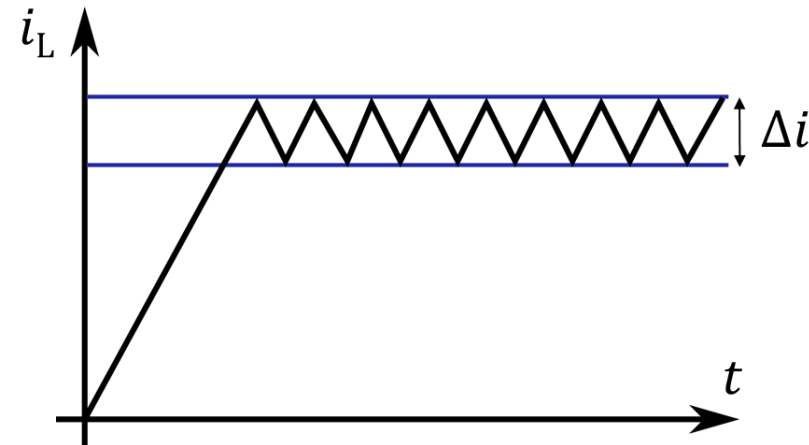
$$di_L = \left( \frac{-V_2}{L} \right) dt$$



Dependent source: Source quantity depends on either 'V' or 'I' existing at some other location in the circuit.

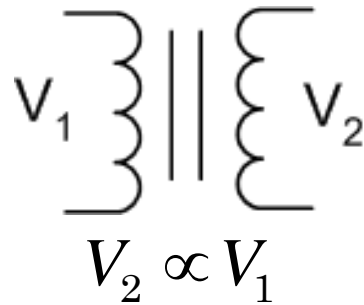
$$V_2 \propto V_1$$

